
Fundamental Experiments in Electrical Engineering / Electronics

1st Edition – type V 0105

© SystemTechnik

Lehr- + Lernmittel GmbH

Altdorfer Strasse 16

88276 Berg / Germany

Phone: + 49 751 / 5 60 75 80

Telefax: + 49 751 / 5 60 75 17

Internet: www.hps-systemtechnik.com

E-mail: export@hps-systemtechnik.com

Order no.: V 0105

All rights reserved. No part of this publication may be reproduced, transmitted, stored in a retrieval system, nor translated into any human or computer language, in any form or by any means, electronic, mechanical, magnetic, optical, chemical, manual or otherwise, without the prior permission of hps SystemTechnik.

0.6.2

Contents

| | | |
|------------|---|----|
| 1. | Electrical Circuit | 1 |
| 2. | Ohm's Law | 7 |
| 3. | Voltage Error Circuit and Current Error Circuit | 11 |
| 4. | Electrical Resistors | 13 |
| 4.1 | Introduction | 13 |
| 4.2 | Linear Resistor | 15 |
| 4.3 | NTC Resistor (Thermistor) | 17 |
| 4.4 | PTC Resistor | 19 |
| 4.5 | Light-dependent Resistor (LDR) | 21 |
| 4.6 | Series Circuiting of Resistors | 23 |
| 4.7 | Parallel Circuiting of Resistors | 25 |
| 4.8 | Mixed Series and Parallel Circuiting | 27 |
| 4.9 | Unloaded Voltage Divider | 29 |
| 4.10 | Loaded Voltage Divider | 31 |
| 5. | Equivalent Voltage Source | 33 |
| 6. | Series Circuiting of Voltage Sources | 37 |
| 7. | Parallel Circuiting of Voltage Sources | 39 |
| 8. | Electrical Power and Work | 41 |
| 9. | Efficiency of Electrical Power | 45 |
| 10. | Voltage, Current and Power Matching | 47 |
| 11. | Establishing and Displaying Characteristics in AC Technology | 49 |
| 11.1 | Introduction | 49 |
| 11.2 | Characteristics of the Sine-Wave Voltage | 49 |
| 11.3 | Active Power with Sine-Wave Voltage | 53 |
| 11.4 | Characteristics of Square-Wave AC Voltage | 57 |

| | | |
|------------|---|------------|
| 12. | Three-Phase Alternating Current | 61 |
| 12.1 | Introduction | 61 |
| 12.2 | Potential Gradient in Three-Phase Current Systems | 63 |
| 12.3 | Loads in Star Circuit | 67 |
| 12.4 | Loads in Delta Circuit | 71 |
| 12.5 | Measurements on a Defective Star Circuit | 75 |
| 12.6 | Measurements on a Defective Delta Circuit. | 79 |
| 13. | Capacitor in the AC Circuit | 83 |
| 13.1 | Introduction | 83 |
| 13.2 | Charging and Discharging Process of a Capacitor | 85 |
| 13.3 | Phase Shift between Current and Voltage on the Capacitor. | 89 |
| 13.4 | Capacitive Reactance of a Capacitor | 91 |
| 13.5 | Series Circuiting of Capacitors. | 93 |
| 13.6 | Parallel Circuiting of Capacitors | 95 |
| 13.7 | Reactive Power of a Capacitor | 97 |
| 14. | Coil in the AC Circuit | 101 |
| 14.1 | Introduction | 101 |
| 14.2 | Switch-On and Switch-Off Process of a Coil | 103 |
| 14.3 | Phase Shift between Current and Voltage on a Coil | 107 |
| 14.4 | Inductive Reactance of a Coil | 109 |
| 14.5 | Series Circuiting of Coils | 111 |
| 14.6 | Parallel Circuiting of Coils | 113 |
| 14.7 | Reactive Power of a Coil. | 115 |
| 15. | Interconnecting Resistor, Capacitor and Coil. | 119 |
| 15.1 | Introduction | 119 |
| 15.2 | Series Circuiting of Resistor and Capacitor. | 119 |
| 15.3 | Parallel Circuiting of Resistor and Capacitor | 123 |
| 15.4 | Series Circuiting of Resistor and Coil | 127 |

| | | |
|------------|--|------------|
| 15.5 | Parallel Circuiting of Resistor and Coil | 131 |
| 15.6 | Series Circuiting of Capacitor and Coil | 135 |
| 15.7 | Parallel Circuiting of Capacitor and Coil | 139 |
| 15.8 | Series Circuiting of Resistor, Capacitor and Coil | 143 |
| 15.9 | Parallel Circuiting of Resistor, Capacitor and Coil | 147 |
| 15.10 | Active, Reactive and Apparent Power | 151 |
| 16. | Transformers | 155 |
| 16.1 | Introduction | 155 |
| 16.2 | Coupling Factor | 155 |
| 16.3 | Transformation Ratio. | 157 |
| 16.4 | Resistance Transformation | 159 |
| 17. | Diodes | 161 |
| 17.1 | Effect of the p-n junction in diodes. | 161 |
| 17.2 | Representation of characteristics of diodes of different semiconductor materials | 163 |
| 17.3 | Half-wave rectifier circuit M1 | 165 |
| 17.4 | On-state and off-state characteristics of Zener diodes | 169 |
| 17.5 | DC voltage-limiting with Zener diodes | 171 |
| 17.6 | Voltage stabilization with Zener diodes. | 177 |
| 17.7 | LEDs | 179 |
| 18. | Transistors | 183 |
| 18.1 | Testing the layers and the rectifying behaviour of bipolar transistors | 183 |
| 18.2 | Current distribution in the transistor and control effect of the base current | 187 |
| 18.3 | Characteristics of the transistor | 191 |
| 18.4 | Influence of the load resistance on the transistor properties. | 196 |
| 18.5 | Basic amplifier circuits with bipolar transistors. | 201 |
| 18.6 | Current controller with transistor | 206 |
| 18.7 | Phase inverter with transistor. | 209 |
| 18.8 | Sine wave generator with RC element | 211 |

| | | |
|------------|--|------------|
| 19. | Thyristors | 213 |
| 19.1 | Triode thyristors (thyristor) | 213 |
| 19.2 | DC voltage switch with thyristors | 218 |
| 20. | Operational Amplifiers | 221 |
| 20.1 | Operational amplifier as inverting amplifier | 221 |
| 20.2 | Operational amplifier as non-inverting amplifier | 225 |
| 20.3 | Operational amplifier as summing amplifier | 288 |
| 20.4 | Operational amplifier as differential amplifier | 233 |
| 20.5 | Dynamic behaviour of the operational amplifier | 237 |

Solutions

| | | |
|-----|--|------|
| 1. | Electrical Circuit | S 1 |
| 2. | Ohm's Law | S 2 |
| 3. | Current Error Circuit and Voltage Error Circuit. | S 4 |
| 4. | Electrical Resistors | S 5 |
| 5. | Equivalent Voltage Source | S 17 |
| 6. | Series Circuiting of Voltage Sources. | S 18 |
| 7. | Parallel Circuiting of Voltage Sources | S 19 |
| 8. | Electrical Power and Work | S 21 |
| 9. | Efficiency of Electrical Power | S 23 |
| 10. | Voltage, Current and Power Matching. | S 24 |
| 11. | Establishing and Displaying Characteristics in AC Technology | S 27 |
| 12. | Three-Phase Alternating Current | S 31 |
| 13. | Capacitor in the AC Circuit. | S 37 |
| 14. | Coil in the AC Circuit | S 45 |
| 15. | Interconnecting Resistor, Capacitor and Coil | S 51 |
| 16. | Transformers | S 61 |
| 17. | Diodes | S 63 |

| | | |
|-----|----------------------------------|------|
| 18. | Transistors | S 73 |
| 19. | Thyristors | S 91 |
| 20. | Operational Amplifiers | S 95 |

Appendix

| | |
|--|-----|
| List of abbreviations and symbols. | A 1 |
| List of plug-in components. | A 5 |
| Required voltage supplies and measuring instruments. | A 7 |

Foil

| | |
|---|-----|
| Front view of the AC/DC BOARD (Type 1017) | F 1 |
|---|-----|