

Transformer Circuits

1- and 3-phase

1st Edition – type V 0171

© hps SystemTechnik

Lehr- + Lernmittel GmbH

Altdorfer Strasse 16
88276 Berg / Germany

Telephone: (07 51) 5 60 75 80
Telefax: (07 51) 5 60 75 17
Internet: <http://www.hps-systemtechnik.com>
E-mail: export@hps-systemtechnik.com

Order no.: V 0171

All rights including those for the translation reserved. This document may not be reproduced in any form (printing, copying or any other form) in whole or in part without the express written permission of hps SystemTechnik or processed, duplicated or distributed using electronic systems.
This does not affect the exceptions expressly mentioned in §§ 53, 54 copyright.

Contents

| | |
|---|----|
| 1 Important Things Worth Knowing about Transformers..... | 1 |
| 1.1 Overview of transformers and their applications | 1 |
| 1.2 Principle structure of transformers | 2 |
| 1.2.1 Structure of the core | 2 |
| 1.2.2 Structure of the windings | 3 |
| 1.3 The rating plate as user information | 4 |
| 1.4 Transformer protection devices..... | 5 |
| 1.4.1 Safety fuses | 5 |
| 1.4.2 Temperature full protection..... | 5 |
| 1.4.3 Thermometer | 5 |
| 1.4.4 Buchholz protection | 6 |
| 1.5 Operating behaviour of transformers..... | 7 |
| 1.5.1 Operating behaviour on no-load | 7 |
| 1.5.2 No-load voltage and no-load current | 7 |
| 1.5.3 Operating behaviour on load..... | 7 |
| 1.5.4 Simplified equivalent circuit diagram and pointer diagram on load..... | 8 |
| 1.5.5 Types of load | 9 |
| 1.6 Switch on and switch off behaviour of a transformer..... | 10 |
| 1.6.1 Switch on behaviour..... | 10 |
| 1.6.2 Switch off behaviour | 10 |
| 1.7 Short-circuit voltage | 11 |
| 1.8 Constructional influence on the short-circuit voltage | 12 |
| 1.9 Short-circuit current | 13 |
| 1.10 Efficiency of transformers | 14 |
| 1.11 Parallel circuit of transformers | 15 |
| 1.12 Proof of the necessity of transformers | 16 |
| 2 1-Phase Transformer..... | 17 |
| 2.1 No-load voltage..... | 17 |
| 2.1.1 No-load voltage of the TRANSFORMER BOARD | 18 |
| 2.2 Transmission ratio | 20 |
| 2.2.1 Transmission ratio of the TRANSFORMER BOARD | 21 |
| 2.3 Current and voltage ratios | 23 |
| 2.3.1 Current and voltage ratios on load | 24 |
| 2.4 Equivalent circuit diagram | 26 |
| 2.4.1 The ideal transformer | 26 |
| 2.4.2 The influence of copper losses..... | 26 |
| 2.4.3 Determining the equivalent resistance..... | 27 |
| 2.4.4 The influence of dispersion..... | 28 |
| 2.4.5 The influence of iron losses | 28 |
| 2.5 No-load characteristic..... | 29 |
| 2.6 No-load losses | 30 |
| 2.7 Short-circuit experiment (only possible with regulating transformer)..... | 31 |
| 3 Auto-Transformer..... | 33 |
| 3.1 Down transformation of voltages | 34 |
| 3.1.1 Auto-transformer on no-load..... | 34 |
| 3.1.2 Auto-transformer on load | 36 |

| | |
|--|-----------|
| 3.2 Up transformation of voltages..... | 38 |
| 3.2.1 Auto-transformer on no-load | 38 |
| 3.2.2 Auto-transformer on load | 39 |
| 4 3-Phase Transformer..... | 40 |
| 4.1 Three-phase current system..... | 40 |
| 4.2 Principle structure of 3-phase transformers | 41 |
| 4.3 Circuit types and names | 42 |
| 4.4 Switching groups | 43 |
| 4.5 Determining the code number | 44 |
| 4.6 Fusing of the 3-phase transformer | 46 |
| 4.7 Switching group Yy | 47 |
| 4.7.1 Switching group and code number | 47 |
| 4.7.2 Behaviour of the Yy0-circuit on symmetrical load | 48 |
| 4.7.3 Behaviour of the Yy0-circuit on asymmetrical load | 50 |
| 4.7.3.1 Single-strand loading of the Yy0-circuit..... | 50 |
| 4.7.3.2 Two-strand loading of the Yy0-circuit..... | 52 |
| 4.7.3.3 Single-strand loading of the YNy0-circuit..... | 54 |
| 4.7.3.4 Two-strand loading of the YNy0-circuit | 56 |
| 4.8.1 Switching group and code number | 58 |
| 4.8.2 Behaviour of the Yd5-circuit on symmetrical load | 59 |
| 4.8.3 Behaviour of the Yd5-circuit on asymmetrical load | 61 |
| 4.8.4 Behaviour of the YNd5-circuit on asymmetrical load | 63 |
| 4.9 Switching group Yz | 65 |
| 4.9.1 Switching group and code number | 65 |
| 4.9.2 Behaviour of the Yz5-circuit on symmetrical load | 66 |
| 4.9.3 Behaviour of the Yz5-circuit on asymmetrical load | 68 |
| 4.9.3.1 Single-strand loading of the Yz5-circuit..... | 68 |
| 4.9.3.2 Two-strand loading of the Yz5-circuit..... | 70 |
| 4.9.3.3 Single-strand loading of the YNz5-circuit..... | 72 |
| 4.9.3.4 Two-strand loading of the YNz5-circuit | 74 |
| 4.10 Switching group Dy | 77 |
| 4.10.1 Switching group and code number | 77 |
| 4.10.2 Behaviour of the Dy5-circuit on symmetrical load | 78 |
| 4.10.3 Behaviour of the Dy5-circuit on asymmetrical load | 80 |
| 4.10.3.1 Single-strand loading of the Dy5-circuit..... | 80 |
| 4.10.3.2 Two-strand loading of the Dy5-circuit | 82 |
| 4.11 Special circuits | 84 |
| 4.11.1 Switching group Dd | 84 |
| 4.11.2 Switching group Dz | 85 |
| 4.11.3 Phase multiplier circuit..... | 86 |
| Solutions | |
| Overhead | F1 |