

**Experiments with the
Four Quadrant Drive**

2nd Edition – Type V 0015



hps SystemTechnik

© **hps SystemTechnik**

Lehr- + Lernmittel GmbH

Altdorfer Strasse 16

88276 Berg (Germany)

Phone: +49 7 51 / 5 60 75-80

Fax: +49 7 51 / 5 60 75 17

Web: <http://www.hps-SystemTechnik.com>

E-mail: export@hps-systemtechnik.com

Order no.: V 0015

All rights reserved. No part of this publication may be reproduced, transmitted, stored in a retrieval system, nor translated into any human or computer language, in any form or by any means, electronic, mechanical, magnetic, optical, chemical, manual or otherwise, without the prior permission of hps SystemTechnik.

Contents

1 Fundamental Principles	1
1.1 The shunt-wound DC machine.....	1
1.1.1 Structure of the machine	1
1.1.2 Operating behaviour as a motor.....	1
1.1.3 Operating behaviour as a generator.....	2
1.1.3.1 The externally excited shunt-wound generator	2
1.1.3.2 The self-excited shunt-wound generator.....	2
1.1.4 Starting up the machine	2
1.1.5 Connecting the machine.....	3
1.2 Current converter systems for adjusting the speed of DC machines.....	4
1.2.1 General information.....	4
1.2.2 The uncontrolled rectifier.....	4
1.2.2.1 The uncontrolled double-pulse bridge circuit B2U	4
1.2.2.2 The uncontrolled six-pulse bridge circuit B6U.....	5
1.2.3 The controlled rectifier.....	6
1.2.3.1 The controlled single-pulse mid-point circuit M1C	6
1.2.3.2 The controlled double-pulse bridge circuit B2C	8
1.2.3.3 The controlled six-pulse bridge circuit B6C.....	10
1.2.4 Inverter stability	12
1.2.5 Current converter drives with DC machines in four-quadrant operation	12
1.2.6 Current converter drives without circuit current.....	13
1.2.7 Current converter drives with circuit current.....	13
1.3 The Four Quadrant Drive (Type 5255) from hps.....	14
1.3.1 General.....	14
1.3.2 The power unit.....	14
1.3.3 The firing components.....	15
1.3.4 The block-up logic	15
1.3.5 The speed controller.....	15
1.3.6 The current controllers 1 and 2	16
1.3.7 The release signal	16
1.3.8 Generation of the field voltage.....	16
2 Introduction for Conducting the Experiments	17
2.1 Auxiliary equipment required from hps SystemTechnik	17
2.1.1 DC Brake Unit (Type 2718)	17
2.1.2 Universal Power Supply (Type 2740.1)	17
2.1.3 Shunt-Wound DC Machine (Type 2701)	17
2.1.4 Isolation Amplifier (Type 8630).....	17
2.1.5 Load (Type 5512)	18
2.1.6 Speed Indicator (Type 5511.1).....	18
2.2 Safety instructions.....	18
2.2.1 General safety instructions.....	18
2.2.2 Safety instructions for the Four Quadrant Drive (Type 5255).....	18
2.2.3 Safety instructions for the DC Brake Unit (Type 2718) and the Shunt-Wound DC Machine (Type 2701)	18
2.2.4 Safety instructions for the Universal Power Supply (Type 2740.1)	19
2.2.5 Safety instructions for the Isolation Amplifier (Type 8630)	19
2.3 Putting into operation	19
2.3.1 General	19
2.3.2 Setting the currents $I_{\max. 1}$ and $I_{\max. 2}$ of the Four Quadrant Drive (Type 5255)	20

2.3.3	Offset adjustment for the speed controller of the Four Quadrant Drive (Type 5255) .21	
2.3.4	Setting the maximum speed n_{max} of the Four Quadrant Drive (Type 5255)	21
3	Experiments with the Four-Quadrant Drive (Type 5255)	23
3.1	Determining the field voltage.....	23
3.2	Determining the synchronization signal.....	25
3.3	Determining the firing pulses in operation without circuit current.....	27
3.4	Determining the firing pulses in operation with circuit current.....	31
3.5	Speed characteristic of the tachogenerator	35
3.6	Voltage and current curves with ohmic loading of a thyristor bridge.....	38
3.7	Mean value of armature voltage and speed with ohmic inductive loading in operation without circuit current	43
3.8	Mean value of armature voltage and speed with ohmic inductive loading in operation with circuit current	47
3.9	Maximum motor speeds in operation without circuit current at different controller settings....	51
3.10	Maximum motor speeds in operation with circuit current at different controller settings	54
3.11	Behaviour at speed jumps with load and different controller settings	57
3.12	Transition from motor to generator mode	61
3.13	Transition from motor to generator mode with change in the direction of rotation.....	64
4	Solutions section	S1
4.1	Solutions to chapter 2.3.2.....	S1
4.2	Solutions to chapter 3.1.....	S2
4.3	Solutions to chapter 3.2.....	S3
4.4	Solutions to chapter 3.3.....	S4
4.5	Solutions to chapter 3.4.....	S7
4.6	Solutions to chapter 3.5.....	S10
4.7	Solutions to chapter 3.6.....	S11
4.8	Solutions to chapter 3.7.....	S19
4.9	Solutions to chapter 3.8.....	S21
4.10	Solutions to chapter 3.9.....	S23
4.11	Solutions to chapter 3.10.....	S24
4.12	Solutions to chapter 3.11.....	S25
4.13	Solutions to chapter 3.12.....	S29
4.14	Solutions to chapter 3.13.....	S30
5	Appendix	A1
5.1	Abbreviations and formula symbols	A1
5.3	Correlation matrix.....	A2
	Overheads	O1